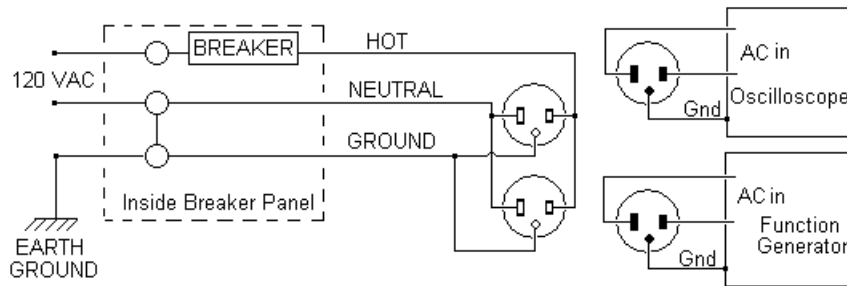


Experiment 41: Three Phase Power / Wye Connection

Introduction

This lab experiment requires a low-voltage 3-phase voltage source that can supply a 12V peak-to-peak sine wave at a current of at least 25mA rms per phase. One can be built on a breadboard as described in Appendix 2. A compact plug-in version of this 3-phase source is described in this lab experiment and also in Appendix 2.

The neutral connection of this source shares the same ground as the lab power supply, function generator, and oscilloscope. Therefore care must be taken to not ground a phase output, such as would occur if the ground lead of the oscilloscope were connected to one of the phase outputs. Study the diagram of a typical 120 VAC single-phase power system below. The grounds of the oscilloscope and function generator are connected together through the ground of the AC receptacles.



Note that the wide connector on the receptacle and the ground connector are connected together and to earth ground at the breaker panel. So the function generator and oscilloscope grounds are connected together through the AC power outlets.

This exercise involves the measurement of the magnitude and phase angles of voltages and currents in a 4-wire and 3-wire, 3-phase, wye connected power system. The effect of balanced and unbalanced loads with and without the neutral wire is measured.

Procedure

Equipment and Parts

Function Generator, Power Supply, 3-Phase Source, Oscilloscope, and Breadboard.
Resistors: Four 100Ω, Four 470Ω, ¼ watt, 5%.

Part A: Balanced Load

1. Measure the values of your resistors (refer to the diagram on the next page) and record:



R1		RA	
R2		RB	
R3		RC	
RG		RX	

If you already have a 3-phase voltage source, set it to produce a 60Hz, 12V peak-to-peak, sine wave per phase, as measured from each line output to neutral. The reference phase will be P0 in this experiment. The phase angle of P1 will be 120° with reference to P0 and the phase angle of P2 will be -120° with reference to P0.

Check that the voltages and phase angles of the 3-phase source are correct.

- If you don't already have a 3-phase voltage source, you can build the circuit described in appendix 2, or use a pc board version of the circuit, the *Phase Tripler*, or the *Phase Tripler II*, which are also described in appendix 2.

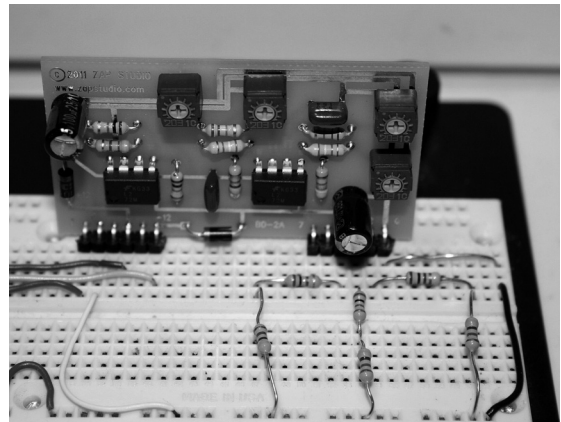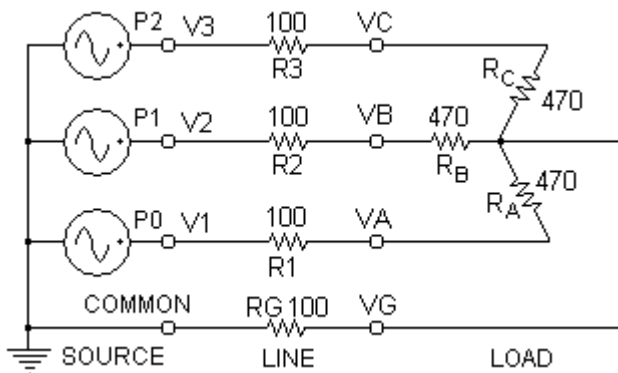Connect the circuit as shown below. The circuit connected on a breadboard with the *Phase Tripler II* is shown on the right.



If you are using the *Phase Tripler II* board, handle it by the edges and carefully insert it into the breadboard. Connect the power supply ground and function generator ground to pin 2, function generator signal to pin 1, +12VDC to pin 4, and -12VDC to pin 6.

Connect the output pins to the circuit. Pin 9 is P0, pin 10 is P1, pin 11 is P2, and P12 is neutral (ground). Also connect the oscilloscope grounds to pin 12.

If you are using the *Phase Tripler*, the same inputs are required except banana binding posts are used for the DC inputs and phase outputs. The function generator is connected to the BNC.

- Connect channel 1 of the oscilloscope to P0 and set the trigger to channel 1. Set the function generator amplitude to produce a 12V peak-to-peak sine wave with no offset on channel 1.
- Connect channel 2 of the oscilloscope to P1. Check that the amplitude is exactly 12V peak-to-peak and that the phase is leading channel 1 by exactly 120° .
- Connect channel 2 of the oscilloscope to P2. Check that the amplitude is exactly 12V peak-to-peak and that the phase is lagging channel 1 by exactly 120° .

[Refer to the calibration procedure in Appendix 2 if steps 3 and 4 don't check.]

If you are using a different 3-phase source, record the magnitude and phase angle of the voltage supplying phases A, B, and C of the load circuit.

6. Measure the magnitude and phase angle of the voltages V_G , V_A , V_B , and V_C with channel 2. Record results below.


Step 6	V_G	V_A	V_B	V_C
Magnitude p-p				
Phase, Deg.				

7. Open the neutral line by removing the 100Ω resistor between the phase tripler ground and node V_G .
8. Measure the magnitudes and phase angles of the voltages V_G , V_A , V_B , and V_C with the oscilloscope channel 2 and record results in the table below.

Step 8	V_G	V_A	V_B	V_C
Magnitude p-p				
Phase, Deg.				

Part B: Unbalanced Load

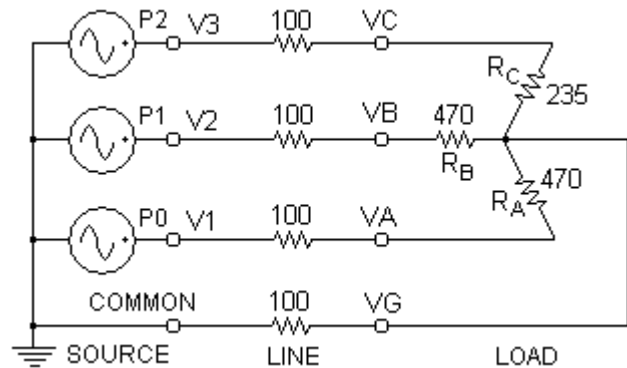1. Connect a 470Ω resistor (R_X) in parallel with R_C so that the R_C branch becomes 235Ω , as shown on the right. Reconnect the 100Ω resistor between node V_G and COMMON.
2. Measure the magnitudes and phase angles of the voltages V_G , V_A , V_B , and V_C with oscilloscope channel 2 and record results in the table below.



Step 2	V_G	V_A	V_B	V_C
Magnitude p-p				
Phase, Deg.				

3. Open the neutral line by removing the 100Ω resistor between the phase tripler ground and node V_G .
4. Measure the magnitude and phase angle of the voltages at nodes n_G , n_A , n_B , and n_C with the oscilloscope channel 2 and record results in the table below.

Step 4	V_G	V_A	V_B	V_C
Magnitude p-p				
Phase, Deg.				

Analysis, Part A

1. Use your measured resistor values and the node voltage method to calculate the voltage V_G for the circuit used in procedure part A. Use the result to calculate the current supplied by the source for each phase (both magnitude and phase angle).
2. Calculate the magnitudes and phases angles of the voltages V_A , V_B , and V_C . Calculate the neutral wire current.
3. Calculate the percent error between the measured and calculated values of the voltage magnitudes V_A , V_B , and V_C . Calculate the absolute error between the phase angles.

Analysis, Part B

1. Use LTspice to simulate the unbalanced circuit with and without the neutral connection. Refer to the example below.
2. Calculate the percent error between the measured and simulated values of the voltage magnitudes V_A , V_B , and V_C . Calculate the absolute error between the phase angles.
3. Use Kirchhoff's current law to show that the neutral wire current is the result of the unbalance of the phase currents.


LTspice 3-Phase Analysis

Three phase circuits can be simulated using three voltage sources. Right click on each source and set their AC Amplitude and phase angle.

Use AC analysis with the start and stop frequencies set to 60Hz and the number of points set to 1.

Use your measured resistor values for your simulation.

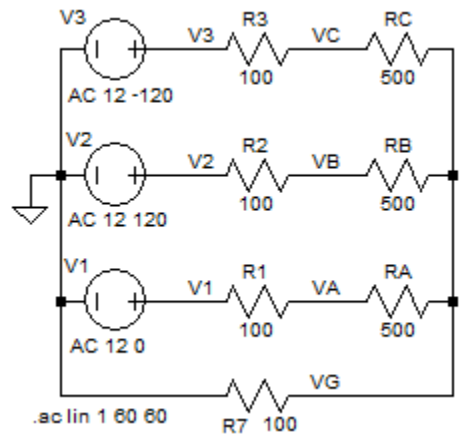The results of simulating the circuit on the right are given below. Verify for yourself that the current supplied by each source is 20mA p-p.



--- AC Analysis ---

frequency:	60	Hz		
V(vc):	mag:	10	phase:	-120° voltage
V(v3):	mag:	12	phase:	-120° voltage
V(vb):	mag:	10	phase:	120° voltage
V(v2):	mag:	12	phase:	120° voltage
V(va):	mag:	10	phase:	6.36111e-016° voltage
V(v1):	mag:	12	phase:	0° voltage